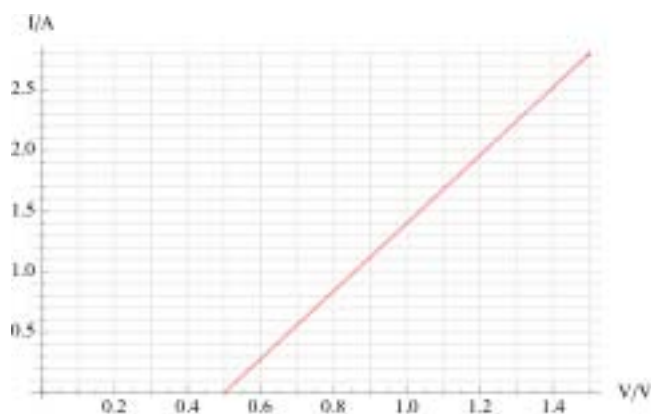


Extension Worksheet – Topic 5, Worksheet 1

- 1 A cylindrical wire of radius r and length L has resistance R . Calculate, in terms of R , the resistance of a wire of the same material with double the radius and double the length. [2]
- 2 The resistivity of a copper is $1.68 \times 10^{-8} \Omega \text{ m}$. Calculate the length of a cylindrical copper wire of resistance 12Ω and radius $2.35 \times 10^{-3} \text{ m}$. [2]
- 3 Show that the current in a wire of cross-sectional area A is given by the expression $I = nevA$ where v is the drift speed of the electrons and n is the number of free electrons per unit volume. [3]
- 4 Electrons leave a metallic surface of area A at a rate of R electrons per unit time per unit area. The average electron speed is v . Deduce that the current leaving the surface is $I = ReA$ and is thus independent of the electron speed. [2]
- 5 The graph shows the variation with applied voltage V (in V) of the current I (in A) in a device.



- a Explain why the device is not ohmic. [1]
- b Determine whether the resistance of the device increases or decreases as the voltage increases past 0.5 V. [2]
- 6 Define the electromotive force (emf) of a battery. [1]
- 7 A battery has negligible internal resistance and emf ϵ . The battery is connected in series to two resistors. The potential difference across the resistors is V_1 and V_2 . The total current leaving the battery is I .
 - a State an expression, in terms of the symbols given, for the total power delivered by the battery. [1]
 - b State expressions for the power dissipated in each of the resistors. [1]
 - c Deduce that $\epsilon = V_1 + V_2$. [1]
 - d The two resistors have resistance R_1 and R_2 . Use the result in c to deduce that the total (effective) resistance of the two resistors in series is $R_1 + R_2$. [2]

- 8** A battery has negligible internal resistance and emf. The battery is connected in parallel to two resistors of resistance R_1 and R_2 .
- a** State an expression for the current in each of the resistors. [1]
- b** Deduce that the total (effective) resistance R of the two resistors in parallel is given by $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$. [2]
- 9** The current I (in A) in a certain device D varies with applied voltage V (in V) at the ends of the device according to the graph below.



- a** Explain how it may be deduced that the device does not obey Ohm's law. [1]
- b** Assuming the device is a filament lamp, explain the shape of this graph. [3]
- c** On the same axes draw a graph to show the variation with applied voltage of the current in another device that has a constant resistance of $25\ \Omega$. [1]
- d** A battery of emf 0.90 V and negligible internal resistance is connected in series to the two devices above. Estimate the current leaving the battery. [2]
- 10** The potential difference across a device is V and the current through it is I .
- a** State an expression for the work that must be done to move a quantity of charge Q across the device. [1]
- b** Use your answer to **a** to derive an expression for the power dissipated in the device. [1]