

Mark scheme for Extension Worksheet – Topic 5, Worksheet 1

- 1 From $R = \rho \frac{L}{A}$ we have that $R = \rho \frac{L}{\pi r^2}$. Hence $R' = \rho \frac{2L}{\pi(2r)^2} = \rho \frac{2L}{4\pi r^2}$; i.e.

$$R' = \frac{2}{4} \left(\rho \frac{L}{\pi r^2} \right) = \frac{R}{2} \quad [2]$$

- 2 $R = \rho \frac{L}{\pi r^2}$ and so $L = \frac{R\pi r^2}{\rho}$; $L = \frac{12 \times \pi (2.35 \times 10^{-3})^2}{1.68 \times 10^{-8}} = 1.2 \times 10^4 \text{ m}$ [2]

- 3 The electrons that will be able to cross the dotted line in the diagram below are those electrons that are at most a distance $v\Delta t$ from the line; the number of these electrons is equal to the number of electrons per unit volume times the volume i.e. $nV = nAv\Delta t$ and so the charge that will cross the dotted line is $\Delta Q = enAv\Delta t$; the current is then

$$I = \frac{\Delta Q}{\Delta t} = \frac{enAv\Delta t}{\Delta t} = enAv;$$



[3]

- 4 In a time of 1 second the number of electrons that will leave the area A is RA ; and so the charge that leaves the surface in 1 second, i.e. the current is $I = RAe$. [2]

- 5 a The graph for an ohmic device would be a straight line **through the origin**, which is not the case here. [1]

- b One way to answer the question is to choose two points say for $V = 0.8 \text{ V}$ and

$$V = 1.2 \text{ V} \text{ and find the resistance in each case: so } R_1 = \frac{0.80}{0.85} = 0.94 \Omega \text{ and}$$

$$R_2 = \frac{1.20}{2.0} = 0.60 \Omega; \text{ so decreases} \quad [2]$$

- 6 The work per unit charge done to move charge completely around a circuit/the power per unit current generated by a battery in a circuit. [1]

- 7 a $\mathcal{E}I$ [1]

- b V_1I and V_2I [1]

- c By energy conservation $\mathcal{E}I = V_1I + V_2I$, hence the result. [1]

- d If the total resistance is R_T we expect that $\mathcal{E} = R_T I$, $V_1 = R_1 I$ and $V_2 = R_2 I$; and so $R_T I = R_1 I + R_2 I$ giving the result. [2]


8 a $I_1 = \frac{\mathcal{E}}{R_1}$ and $I_2 = \frac{\mathcal{E}}{R_2}$ [1]

b If R is the total resistance we expect that $I = \frac{\mathcal{E}}{R}$ and $I = I_1 + I_2$; so $\frac{\mathcal{E}}{R} = \frac{\mathcal{E}}{R_1} + \frac{\mathcal{E}}{R_2}$ giving the result. [2]

9 a A device obeying Ohm's law would give a straight line graph through the origin which is not the case here. [1]

b In a filament lamp the resistance is expected to increase as the voltage across it increases; because at higher voltages there would be higher temperatures inside the wire and so greater chance of collisions of electrons with metal atoms; the graph shows that the resistance increases as the voltage increases. [3]

c See graph below:

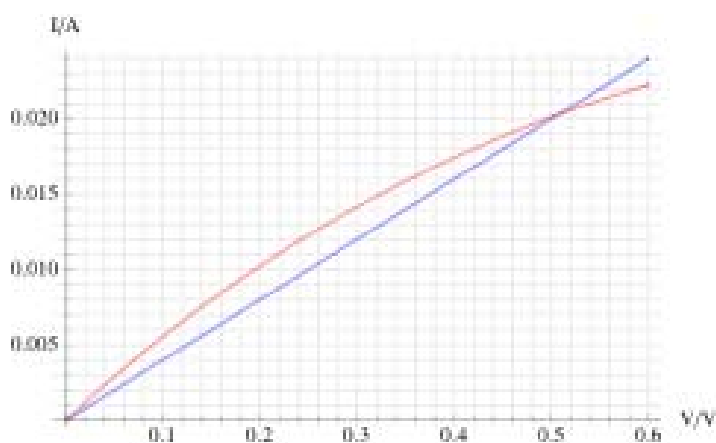

d This requires trial and error to use the graphs and find that current for which the corresponding voltages add up to 0.90 V; the required current is in between 0.018 A and 0.019 A. [2]

10 a The work required is $W = QV$ [1]

b The power is $P = \frac{W}{t} = \frac{QV}{t} = IV$ [1]