

**Mark scheme for Support Worksheet – Topic 5,
Worksheet 1**

- 1** $W = qV = 24 \times 10^{-3} \times 250 = 0.60 \text{ J}$ [1]
- 2** $W = qV \Rightarrow V = \frac{W}{q} = \frac{5.8 \times 10^{-3}}{1.2 \times 10^{-9}} = 4.8 \times 10^6 \text{ V}$ [1]
- 3** Since $W = qV$ and $q = 2e$, $V = 11 \text{ V}$; hence for the electron with $q = e$, $W = 11 \text{ eV}$ [2]
- 4** $W = qV = 1.6 \times 10^{-19} \times 150 = 2.4 \times 10^{-17} \text{ J}$;
 $\frac{1}{2}mv^2 = W \Rightarrow v = \sqrt{\frac{2W}{m}} = \sqrt{\frac{2qV}{m}} = \sqrt{\frac{2 \times 2.4 \times 10^{-17}}{9.1 \times 10^{-31}}}$; $v = 7.3 \times 10^6 \text{ ms}^{-1}$ [3]
- 5** $I = \frac{\Delta Q}{\Delta t} = \frac{1.6 \times 10^{-19} \times 6.8 \times 10^{16}}{1} \text{ A}$; $I = 11 \text{ mA}$ [2]
- 6** **a** $3R = 18.0 \Omega$ [1]
- b** $R + \frac{R}{2} = \frac{3R}{2} = 9.0 \Omega$ [1]
- c** $\frac{1}{R_T} = \frac{1}{2R} + \frac{1}{2R} = \frac{1}{R}$, so $R_T = R = 6.0 \Omega$ [1]
- 7** Each part of the wire has resistance $\frac{R}{2}$; and so the total is given by
 $\frac{1}{R_T} = \frac{1}{\frac{R}{2}} + \frac{1}{\frac{R}{2}} = \frac{4}{R}$ i.e. $R_T = \frac{R}{4}$ [2]
- 8** $R = \frac{\rho L}{A} = 2.2 \times 10^{-6} \times \frac{4.5}{\pi \times (0.24 \times 10^{-3})^2}$; $R = 55 \Omega$ [2]
- 9** The potential difference across the external resistor is $V = \frac{W}{q} = \frac{7.2 \times 10^{-19}}{1.6 \times 10^{-19}} = 4.5 \text{ V}$;
the potential difference across the internal resistor is $V = RI = 0.80 \times 1.5 = 1.2 \text{ V}$; so
the emf is $4.5 + 1.2 = 5.7 \text{ V}$ [3]
- 10** The current leaving the battery is $I = \frac{V}{R} = \frac{5.4}{15} = 0.36 \text{ A}$; the potential difference
across the internal resistor is $6.0 - 5.4 = 0.6 \text{ V}$; hence the internal resistance is
 $r = \frac{V}{I} = \frac{0.6}{0.36} = 1.7 \Omega$ [3]
- 11** The potential difference across the resistor must be $9.0 - 4.5 = 4.5 \text{ V}$; and so the
resistance is $R = \frac{V}{I} = \frac{4.5}{0.15} = 30 \Omega$ [2]