

## Mark scheme for Support Worksheet – Topic 5, Worksheet 2

- 1 a** The potential difference across the single resistor is  
 $V = RI = 12 \times 0.48 = 5.76 \text{ V}$ ; across the other  $12 \Omega$  resistor it is  
 $V = RI = 12 \times 0.36 = 4.32 \text{ V}$  and so the emf is  $5.76 + 4.32 = 10.08 \approx 10 \text{ V}$  [2]
- b** The total power is the emf times the current; and so is  $10.08 \times 0.48 = 4.8 \text{ W}$  [2]
- c** The potential difference across  $R$  is  $4.32 \text{ V}$  and the current through it is  $0.12 \text{ A}$ ;  
 hence the resistance is  $R = \frac{V}{I} = \frac{4.32}{0.12} = 36 \Omega$  [2]
- 2 a** The potential difference across the  $25 \Omega$  resistor (and hence also  $R_2$ ) is  
 $V = RI = 25 \times 0.20 = 5.0 \text{ V}$ ; hence  $R_2 = \frac{V}{I} = \frac{5.0}{0.25} = 20 \Omega$  [2]
- b** The potential difference across the single resistor  $R_1$  is  $12 - 5.0 = 7.0 \text{ V}$  and the  
 current through it is  $0.45 \text{ A}$ ; hence  $R_1 = \frac{V}{I} = \frac{7.0}{0.45} \approx 16 \Omega$  [2]
- 3** The total resistance of the circuit is given by:  $\frac{1}{12} + \frac{1}{12} = \frac{1}{6} \Rightarrow R = 6 \Omega$ . The current is  
 therefore  $I = \frac{12}{6.0} = 2.0 \text{ A}$ ; the potential at the top of the voltmeter is therefore  
 $12 - 4.0 \times 1.0 = 8.0 \text{ V}$  and at the bottom it is  $12 - 8.0 \times 1.0 = 4.0 \text{ V}$ ; the potential  
 difference is therefore  $8.0 - 4.0 = 4.0 \text{ V}$  [3]
- 4 a** The current leaving the battery is  $I = \frac{P}{\varepsilon} = \frac{9.0}{6.0} = 1.5 \text{ A}$ ; the reading of the  
 voltmeter is then  $V = \varepsilon - Ir = 6.0 - 2.0 \times 1.5 = 3.0 \text{ V}$  [2]
- b** the resistance  $R$  is then  $R = \frac{V}{I} = \frac{3.0}{1.5} = 2.0 \Omega$  [1]