

## Mark scheme for Support Worksheet – Topic 5, Worksheet 3

- 1 a** As the intensity of light increases the resistance of the LDR decreases and so the potential difference across it decreases; hence the potential difference across  $R$  increases. [2]
- b** As the temperature increases the resistance of the thermistor decreases and so the potential difference across it decreases; hence the potential difference across  $R$  increases. [2]
- 2 a** The resistance of A decreases as the current increases; and the resistance of B increases. [2]
- b** From the graph the voltages at 2.4 A are  $18\ \Omega$  and  $8.0\ \Omega$ ; so  
 $P_A = 2.4 \times 18 = 43.2 \approx 43\ \text{W}$  and  $P_B = 2.4 \times 8.0 = 19.2 \approx 19\ \text{W}$  [2]
- c** The potential difference across the internal resistor is  $30 - 8.0 - 18 = 4.0\ \text{V}$ ; and  
 so the internal resistance  $r = \frac{V}{I} = \frac{4.0}{2.4} = 1.7\ \Omega$  [2]
- 3 a**  $P = VI$  and so  $I = \frac{P}{V} = \frac{12}{6.0} = 2.0\ \text{A}$  [1]
- b**  $R = \frac{V}{I} = \frac{6.0}{2.0} = 3.0\ \Omega$  [1]
- c** The resistance of AB is  $\frac{2R}{3}$  and that of BC is  $\frac{R}{3}$ . The total resistance of the light bulb and AB must equal that of BC; so  $\frac{3}{2R} + \frac{1}{3} = \frac{9+2R}{6R} \Rightarrow R_T = \frac{6R}{9+2R}$ .  
 $\frac{6R}{9+2R} = \frac{R}{3} \Rightarrow 18 = 9 + 2R \Rightarrow R = 4.5\ \Omega$  [2]
- 4** As the temperature of the thermistor increases its resistance, and hence its potential difference, decreases; therefore the potential difference across the lamp increases; and so does its brightness. [3]