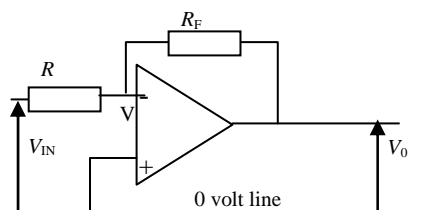



Extension Worksheet – Option F, Worksheet 4, HL only

- 1 The diagram shows an inverting op-amp.




The op-amp operates with a power supply of $\pm 6.0\text{ V}$ and $R_F = 80\text{ k}\Omega$ and $R = 16\text{ k}\Omega$.

- a Determine the closed loop gain of the op-amp. [1]
- b Calculate the output voltage when $V_{\text{IN}} = -0.60\text{ V}$. [2]
- c Calculate the input voltage for which positive saturation is achieved and hence state the output when $V_{\text{IN}} = -2.0\text{ V}$. [2]
- d Determine the current in the R_F resistor when $V_{\text{IN}} = +1.2\text{ V}$. [2]
- e The graph below shows how the input signal varies with time. Sketch a graph to show how the output voltage varies with time.

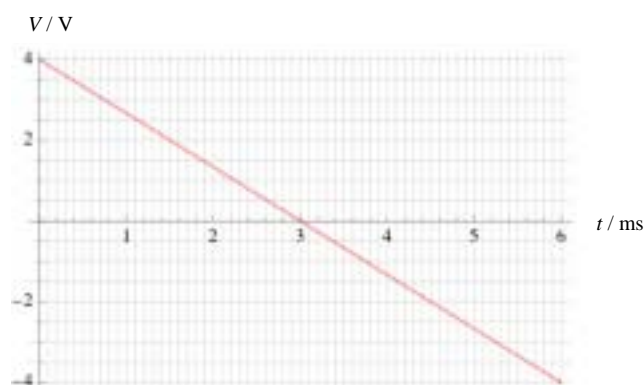

[3]

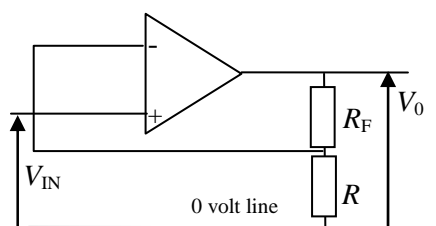- 2 The diagram shows a non-inverting op-amp.



The op-amp operates with a power supply of $\pm 6.0\text{ V}$ and $R_F = 120\text{ k}\Omega$ and $R = 20\text{ k}\Omega$.

- a Determine the closed loop gain of the op-amp. [1]
- b Calculate the output voltage when $V_{\text{IN}} = -0.50\text{ V}$. [2]
- c Calculate the input voltage for which positive saturation is achieved and hence state the output when $V_{\text{in}} = +3.0\text{ V}$. [2]
- 3 Outline the use of the Schmitt trigger in digital signal transmissions. [3]