

## Topic 11 – Practical 2

### *RC circuit – Capacitor charging*

#### Safety

The capacitor should be connected in the circuit with the correct polarity.

#### Apparatus and materials

- batteries or dc power supply
- resistors 10k $\Omega$ , 22k $\Omega$
- capacitors 1000 $\mu$ F, 2200 $\mu$ F
- voltmeter or multimeter
- push-to-make switch
- connecting wires
- stopwatch
- graph paper

#### Introduction

A capacitor is an electrical circuit component that can store electrical charges when connected to a source. When a capacitor is charging, it stores electric energy. Capacitance  $C$  is defined as

$$C = \frac{q}{V}$$


where  $q$  is the charge on each plate of the capacitor and  $V$  the potential difference applied across it.

When a capacitor is connected in series with a resistor and a source, then the amount charge  $q$  on the capacitor at time,  $t$ , after it was connected to the source is given by:

$$q = CV[1 - e^{-t/RC}]$$

where  $C$  is the capacitance of the capacitor,  $V$  is the potential difference provided by the source and  $R$  is the resistance of the resistor. The product  $RC$  is called the time constant and it is a measure of how fast the capacitor is charging.

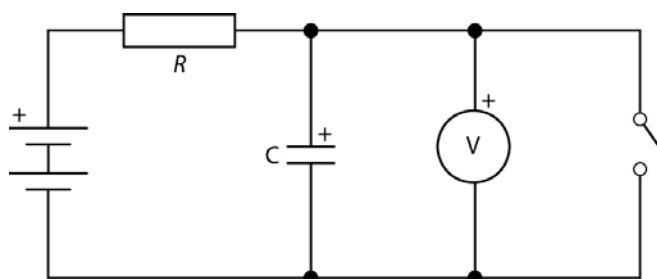In this experiment you will investigate the charging of a capacitor.



#### Procedure

- 1 Construct the circuit shown in the diagram above using  $R = 10\text{ k}\Omega$  and  $C = 1000\text{ }\mu\text{F}$ . The dc power supply should be set to 9V. Be careful to connect the capacitor with the correct polarity.
- 2 Close the switch to completely discharge the capacitor.
- 3 The moment you open the switch the capacitor will start charging and you will consider  $t$  to equal 0 seconds. Using the stopwatch and the voltmeter, measure the potential difference across the capacitor readings every 10 seconds for a total of 3 minutes.

- 4 Record your measurements in a suitable table.
- 5 Repeat the process using  $R = 10 \text{ k}\Omega$  and  $C = 2200 \text{ }\mu\text{F}$ .
- 6 Repeat the process using  $R = 22 \text{ k}\Omega$  and  $C = 1000 \text{ }\mu\text{F}$ .
- 7 Plot graphs of the potential across the capacitor against time for all three combinations of  $RC$  on the same axes.
- 8 From your graphs find the time it takes for the potential difference across the capacitor to reach 63% of its final value. Compare this time with the value of the product  $RC$  (time constant) in each case. Be careful with the units!
- 9 Using the boxes of your graph paper estimate the area between each graph and the x-axis. This area represents the total charge  $q$  on the capacitor after the given time.
- 10 Calculate the capacitance of each capacitor using the formula  $C = \frac{q}{V}$ , where  $V$  is the potential difference across the capacitor at  $t = 3$  minutes. Compare the calculated values with the ones marked on the capacitors you used.

### Questions

- 1 What is the name for the relationship demonstrated by the graph of capacitor potential difference vs time?
- 2 If you wish the capacitor to charge faster, what resistor would you use?